

# Chapter 2 Combinational systems

---

- Definition: combinational logic, block, system
- Logic gates and truth table
- Don't care condition
- switching algebra (Boolean)
- Complement
- Functions with gates

# Digital logic circuits

---

- Digital circuits: hardware components that manipulate binary information
- Logic gates implement logic functions.
- Basic logical operators are the logic functions **AND**, **OR** and **NOT**
- Boolean Algebra: a useful mathematical system for specifying and transforming logic functions.
- We study Boolean algebra as a foundation for designing and analyzing digital systems!
  
- Hierarchical design: circuit design hierarchy (Y-chart)
- Basic circuit element can be
  - Transistor
  - Logic gate
  - Wire

# Levels of abstractions


---

Level	Behavioral forms	Structural components	Physical objects
Transistor	differential equations, current-voltage diagrams	transistors, resistors, capacitors	analog and digital cells
Gate	Boolean equations, finite state machines	gates, flip-flops	modules, units
Register	algorithms, flowcharts, instruction sets	adders, registers, counters, queues	microchips
Processor	executable specification, programs	processors, controllers, memories	printed-circuit boards, multichip modules

# Y chart

## BEHAVIORAL DOMAIN

## STRUCTURAL DOMAIN

 

## PHYSICAL DOMAIN

# Logical operations

---

**The three basic logical operations are:**

**AND**

**OR**

**NOT**

**AND is denoted by a dot ( $\cdot$ )**

**OR is denoted by a plus ( $+$ )**

**NOT is denoted by an overbar ( $\bar{\phantom{x}}$ ), a single quote mark ( $'$ ) after, or ( $\sim$ ) before the variable**

**Examples:**

**$Y = A \cdot B$  is read "Y is equal to A AND B."**

**$Z = X + Y$  is read "z is equal to x OR y."**

**$X = \sim A$  is read "X is equal to NOT A."**

■ **Note: The statement:**

**$1 + 1 = 2$  (read "one plus one equals two")**

**is not the same as**

**$1 + 1 = 1$  (read "1 or 1 equals 1")**

# Operator definition

---

- Operations are defined on the values "0" and "1" for each operator:

## AND

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

## OR

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

## NOT

$$\overline{0} = 1$$

$$\overline{1} = 0$$

# Truth table




- *Truth table* - a tabular listing of the values of a function for all possible combinations of values on its arguments
- Example: Truth tables for the basic logic operations:

A B	$C = A + B$
0 0	0
0 1	1
1 0	1
1 1	1

A B	$C = A \cdot B$
0 0	0
0 1	0
1 0	0
1 1	1

A	$C = \sim A$
0	1
1	0

- symbols

   


# Logic function implementation


## ● Using Switches

- For inputs:
  - logic 1 is switch closed
  - logic 0 is switch open
- For outputs:
  - logic 1 is light on
  - logic 0 is light off.
- NOT uses a switch such that:
  - logic 1 is switch open
  - logic 0 is switch closed


**Switches in parallel => OR**

 

**Switches in series => AND**

 

**Normally-closed switch => NOT**

 



# Logic Diagrams and Expressions

---


## Truth Table

<b>X Y Z</b>	<b><math>F = X + \bar{Y} \times Z</math></b>
<b>0 0 0</b>	<b>0</b>
<b>0 0 1</b>	<b>1</b>
<b>0 1 0</b>	<b>0</b>
<b>0 1 1</b>	<b>0</b>
<b>1 0 0</b>	<b>1</b>
<b>1 0 1</b>	<b>1</b>
<b>1 1 0</b>	<b>1</b>
<b>1 1 1</b>	<b>1</b>

## Equation





 

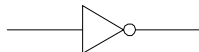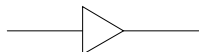
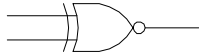
$$F = X + \bar{Y} Z$$

## Logic Diagram



- Boolean equations, truth tables and logic diagrams describe the same function!
- Truth tables are unique; expressions and logic diagrams are not. This gives flexibility in implementing functions.

# Basic logic library

NAME	GRAPHIC SYMBOL	FUNCTIONAL EXPRESSION	COST(NUMBER OF TRANSISTORS)	GATE DELAY(NS)	Truth table															
Inverter		$F = x'$	2	1	<table><tr><td>x</td><td>F</td></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	x	F	0	1	1	0									
x	F																			
0	1																			
1	0																			
Driver		$F = x$	4	2	<table><tr><td>x</td><td>F</td></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	x	F	0	0	1	1									
x	F																			
0	0																			
1	1																			
AND		$F = xy$	6	2.4	<table><tr><td>x</td><td>y</td><td>F</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	0	1	0	0	1	1	1
x	y	F																		
0	0	0																		
0	1	0																		
1	0	0																		
1	1	1																		
OR		$F = x+y$	6	2.4	<table><tr><td>x</td><td>y</td><td>F</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	1
x	y	F																		
0	0	0																		
0	1	1																		
1	0	1																		
1	1	1																		
NAND		$F = (xy)'$	4	1.4	<table><tr><td>x</td><td>y</td><td>F</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	1	1	0	1	1	1	0
x	y	F																		
0	0	1																		
0	1	1																		
1	0	1																		
1	1	0																		
NOR		$F = (x+y)'$	4	1.4	<table><tr><td>x</td><td>y</td><td>F</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	0
x	y	F																		
0	0	1																		
0	1	0																		
1	0	0																		
1	1	0																		
XOR		$F = x\oplus y$	14	4.2	<table><tr><td>x</td><td>y</td><td>F</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	0
x	y	F																		
0	0	0																		
0	1	1																		
1	0	1																		
1	1	0																		
XNOR		$F = x\odot y$	12	3.2	<table><tr><td>x</td><td>y</td><td>F</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	1
x	y	F																		
0	0	1																		
0	1	0																		
1	0	0																		
1	1	1																		

# Design process

---

- **Design process is a sequence of steps which leads from a product concept to manufacturing drawings that show how to build that product**
- **Computer design**
  - **Server, desktop, embedded**
- **System design**
- **ASIC (application specific integrated circuit)**
- **IP blocks (processor, memory, I/O, control units)**

# Switching algebra

---

P1a.	$a + b = b + a$	P1b.	$ab = ba$	Commutative
P2a.	$a + (b + c) = (a + b) + c$	P2b.	$a(bc) = (ab)c$	Associative
P3a.	$a + 0 = a$	P3b.	$a \cdot 1 = a$	Identity
P3aa.	$0 + a = a$	P3bb.	$1 \cdot a = a$	
P4a.	$a + 1 = 1$	P4b.	$a \cdot 0 = 0$	Null
P4aa.	$1 + a = 1$	P4bb.	$0 \cdot a = 0$	
P5a.	$a + a' = 1$	P5b.	$a \cdot a' = 0$	Complement
P5aa.	$a' + a = 1$	P5bb.	$a' \cdot a = 0$	
P6a.	$a + a = a$	P6b.	$a \cdot a = a$	Idempotency
P7.	$(a')' = a$			Involution

# Switching algebra

---

P8a.	$a(b + c) = ab + ac$	P8b.	$a + bc = (a + b)(a + c)$	Distributive
P9a.	$ab + ab' = a$	P9b.	$(a + b)(a + b') = a$	Adjacency
P9aa.	$a'b' + a'b + ab + ab' = 1$	P9bb.	$(a' + b')(a' + b)(a + b)(a + b') = 0$	
P10a.	$a + a'b = a + b$	P10b.	$a(a' + b) = ab$	Simplification
P11a.	$(a + b)' = a'b'$	P11b.	$(ab)' = a' + b'$	DeMorgan
P11aa.	$(a + b + c \dots)' = a'b'c' \dots$	P11bb.	$(abc \dots)' = a' + b' + c' \dots$	
P12a.	$a + ab = a$	P12b.	$a(a + b) = a$	Absorption
P13a.	$at_1 + a't_2 + t_1t_2 = at_1 + a't_2$	P13b.	$(a + t_1)(a' + t_2)(t_1 + t_2) = (a + t_1)(a' + t_2)$	Consensus
P14a.	$ab + a'c = (a + c)(a' + b)$			

# Example 1: Boolean Algebraic Proof

---

- $A + A \cdot B = A$  (Absorption Theorem)

Proof Steps

Justification (identity or theorem)

$$A + A \cdot B$$

$$= A \cdot 1 + A \cdot B$$

$$X = X \cdot 1$$

$$= A \cdot (1 + B)$$

$$X \cdot Y + X \cdot Z = X \cdot (Y + Z) \text{ (Distributive Law)}$$

$$= A \cdot 1$$

$$1 + X = 1$$

$$= A$$

$$X \cdot 1 = X$$

- Our primary reason for doing proofs is to learn:
  - Careful and efficient use of the identities and theorems of Boolean algebra, and
  - How to choose the appropriate identity or theorem to apply to make forward progress, irrespective of the application.

## Example 2: Boolean Algebraic Proofs

---

- $AB + A'C + BC = AB + A'C$  (Consensus Theorem)

Proof Steps

Justification (identity or theorem)

$$AB + A'C + BC$$

$$= AB + A'C + 1 \cdot BC$$

?

$$= AB + A'C + (A + A') \cdot BC$$

?

=

## Example 3: Boolean Algebraic Proofs

---

- $(X+Y)'Z+XY' = Y'(X+Z)$

proof steps    Justification



# Proof of DeMorgan's Laws

---

- $(x+y)' = x'y'$

It is important that we do not USE DeMorgan's Laws in doing this proof. This requires a different proof method. We will show that,  $x' \cdot y'$ , satisfies the definition of the complement of  $(x + y)$ , defined as  $(x + y)'$  by DeMorgan's Law. To show this we need to show that  $A + A' = 1$  and  $A \cdot A' = 0$  with  $A = x + y$  and  $A' = x' \cdot y'$ . This proves that  $x' \cdot y' = (x + y)'$ .

Part 1: Show  $x + y + x' \cdot y' = 1$ .

$$\begin{aligned} & x + y + x' \cdot y' \\ &= (x + y + x') (x + y + y') \\ &= (x + x' + y) (x + y + y') \\ &= (1 + y)(x + 1) \\ &= 1 \cdot 1 \\ &= 1 \end{aligned}$$

$$X + YZ = (X + Y)(X + Z) \text{ (Distributive Law)}$$

$$X + Y = Y + X \text{ (Commutative Law)}$$

$$X + X' = 1$$

$$1 + X = 1$$

$$1 \cdot X = 1$$

Part 2: Show  $(x + y) \cdot x' \cdot y' = 0$ .

$$\begin{aligned} & (x + y) \cdot x' \cdot y' \\ &= (x \cdot x' \cdot y' + y \cdot x' \cdot y') \\ &= (x \cdot x' \cdot y' + y \cdot y' \cdot x') \\ &= (0 \cdot y' + 0 \cdot x') \\ &= (0 + 0) \\ &= 0 \end{aligned}$$

$$X(Y + Z) = XY + XZ \text{ (Distributive Law)}$$

$$XY = YX \text{ (Commutative Law)}$$

$$X \cdot X' = 0$$

$$0 \cdot X = 0$$

$$X + 0 = X \text{ (With } X = 0)$$

# Boolean Function Evaluation

---

$$F1 = xy\bar{z}$$

$$F2 = x + \bar{y}z$$

$$F3 = \bar{x}\bar{y}\bar{z} + \bar{x}yz + x\bar{y}$$

$$F4 = x\bar{y} + \bar{x}z$$

x	y	z	F1	F2	F3	F4
0	0	0	0	0		
0	0	1	0	1		
0	1	0	0	0		
0	1	1	0	0		
1	0	0	0	1		
1	0	1	0	1		
1	1	0	1	1		
1	1	1	0	1		

# Expression Simplification

---

- An application of Boolean algebra
- Simplify to contain the smallest number of literals (complemented and uncomplemented variables):

$$\mathbf{AB + \bar{A}CD + \bar{A}BD + \bar{A}C\bar{D} + ABCD}$$

$$= \mathbf{AB + ABCD + A'CD + A'CD' + A'BD}$$

$$= \mathbf{AB + AB(CD) + A'C (D + D') + A'BD}$$

$$= \mathbf{AB + A'C + A'BD}$$

$$= \mathbf{B(A + A'D) + A'C}$$

$$= \mathbf{B (A + D) + A'C \text{ 5 literals}}$$

# Complementing Functions

---

- Use DeMorgan's Theorem to complement a function:
  1. Interchange AND and OR operators
  2. Complement each constant value and literal
- Examples
  - Complement  $F = x'yz' + xy'z'$
  - Complement  $G = (a' + bc)d' + e$

# Complement example

---

- Example 2.5

$$F = wx'y + xy' + wxz$$

$$F' =$$

- Example 2.6

$$f = ab'(c + d'e) + a'bc'$$

$$f' = [ab'(c + d'e) + a'bc']' \quad \text{using [P11a], [P11b]}$$

$$= [ab'(c + d'e)][a'bc']'$$

$$= [a' + b + (c + d'e)'][a + b' + c]$$

$$= [a' + b + c'(d'e)'][a + b' + c]$$

$$= [a' + b + c'(d + e')][a + b' + c]$$

# Boolean Functions

- Truth Table for  $F_1 = xy + xy'z + x'yz$   
its Complement  $F_1' = (x'+y')(x'+y+z')(x+y'+z')$

	VARIABLE VALUES	FUNCTION VALUES
ROW NUMBER	x y z	F <sub>1</sub> F <sub>1</sub> '
0	0 0 0	0 1
1	0 0 1	0 1
2	0 1 0	0 1
3	0 1 1	1 0
4	1 0 0	0 1
5	1 0 1	1 0
6	1 1 0	1 0
7	1 1 1	1 0

ex)  $F_1 = 1$

➡  $x=1$  and  $y=1$ , or if  $x=1$ ,  $y=0$ , and  $z=1$ ,  
or if  $x=0$ ,  $y=1$ , and  $z=1$ .

- As a general rule, the truth table for any Boolean function of  $n$  variable has  $2^n$  rows.

# Implementation of Functions with AND, OR, and NOT Gates

---

## ■ Block diagram

$$f = x'yz' + x'yz + xy'z' + xyz$$

- Block diagram of  $f$  in sum of standard products form.

 


Figure 2.7 in text

# Canonical Forms - Minterm

## ■ Minterm

- Let  $i = b_{n-1} \dots b_0$  be a binary number
- A minterm of variables  $x_{n-1}, x_{n-2}, \dots, x_0$

$$m_i(x_{n-1}, x_{n-2}, \dots, x_0) = y_{n-1} \dots y_0$$

$$y_k = \begin{cases} x_k & \text{if } b_k = 1 \text{ all } k \text{ } 0 \leq k \leq n-1 \\ x_k' & \text{if } b_k = 0 \end{cases}$$

- All minterms of the three binary variables, x, y, and z

x	y	z	MINTERMS	NOTATION
0	0	0	$x'y'z'$	$m_0$
0	0	1	$x'y'z$	$m_1$
0	1	0	$x'yz'$	$m_2$
0	1	1	$x'yz$	$m_3$
1	0	0	$xy'z'$	$m_4$
1	0	1	$xy'z$	$m_5$
1	1	0	$xyz'$	$m_6$
1	1	1	$xyz$	$m_7$



# Canonical Forms - Minterm

---

$$F_1 = m_3 + m_5 + m_6 + m_7 = x'yz + xy'z + xyz' + xyz \quad 1\text{-minterms}$$

$$F_1' = m_0 + m_1 + m_2 + m_4 = x'y'z' + x'y'z + x'yz' + xy'z' \quad 0\text{-minterms}$$

- An important property of Boolean algebra :  
*Any Boolean function can be expressed as a sum of its 1-minterms.*

- Sum-of-minterms form  
 $F(\text{list of variables}) = \sum (\text{list of 1-minterm indices})$

$$\begin{aligned} \text{ex) } F_1(x,y,z) &= \sum(3,5,6,7) \\ F_1'(x,y,z) &= \sum(0,1,2,4) \end{aligned}$$

# Sum of minterm expressions

## EXAMPLE 3.1 Sum-of-minterms expansion

PROBLEM Express the Boolean function  $F=x+yz$  as a sum of minterms

SOLUTION

$$\begin{aligned} F &= x+yz \\ &= x(y+y')(z+z')+(x+x')yz \\ &= xyz+xy'z+xyz'+xy'z'+xyz+x'yz \end{aligned}$$

After removing duplicates,

$$\begin{aligned} F &= x'yz+xy'z'+xy'z+xyz'+xyz \\ &= m_3 + m_4 + m_5 + m_6 + m_7 \\ &= \sum (3,4,5,6,7) \end{aligned}$$

## EXAMPLE 3.2 Conversion to a sum of minterms

PROBLEM Convert the Boolean function  $F=x+yz$  into a sum of minterms by using a truth table.  
(Table 3.10)

SOLUTION

$$F = m_3 + m_4 + m_5 + m_6 + m_7$$

Truth Table for  
 $F = x + yz$

x	y	z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

# Canonical Forms - Maxterm

- Eight maxterms of the three binary variables, x,y, and z

x	y	z	MAXTERMS	NOTATION
0	0	0	$x + y + z$	$M_0$
0	0	1	$x + y + z'$	$M_1$
0	1	0	$x + y' + z$	$M_2$
0	1	1	$x + y' + z'$	$M_3$
1	0	0	$x' + y + z$	$M_4$
1	0	1	$x' + y + z'$	$M_5$
1	1	0	$x' + y' + z$	$M_6$
1	1	1	$x' + y' + z'$	$M_7$

- The expression for  $F_1 = x'yz + xy'z + xyz' + xyz$   
 $(F_1)' = (x'yz + xy'z + xyz' + xyz)'$   
 $= (x + y' + z')(x' + y + z')(x' + y' + z)(x' + y' + z')$   
 $= M_3 M_5 M_6 M_7$

Similarly, by complementing the expression

$$\begin{aligned}
 F_1 &= (F_1')' \\
 &= (x'y'z' + x'y'z + x'yz' + xy'z')' \\
 &= (x + y + z)(x + y + z')(x + y' + z)(x' + y + z) \\
 &= M_0 M_1 M_2 M_4
 \end{aligned}$$

# Product of maxterm

---

- An second unique property of Boolean algebra :  
*Any Boolean function can be expressed as a product of its 0-maxterms.*
- **Product of maxterms** form
$$F(\text{list of variables}) = \prod (\text{list of 0-maxterm indices})$$
- A general conversion procedure to convert from one canonical form to another, interchange the symbols  $\sum$  and  $\prod$ , and list the numbers that were excluded from the original form.

## **EXAMPLE 3.3** Product-of-maxterms expansion

**PROBLEM** Derive the product-of-maxterms form for the Boolean function

$$F = x'y' + xz$$

**SOLUTION**

$$\begin{aligned} F &= x'y' + xz \\ &= (x'y' + x)(x'y' + z) \\ &= (x' + x)(y' + x)(x' + z)(y' + z) \\ &= (x + y')(x' + z)(y' + z) \end{aligned}$$

# Product of maxterm

into two maxterms

$$x+y' = x+y'+zz' = (x+y'+z)(x+y'+z')$$

$$x'+z = x'+z+yy' = (x'+y+z)(x'+y'+z)$$

$$y'+z = y'+z+xx' = (x+y'+z)(x'+y'+z)$$

Finally,

$$\begin{aligned} F &= (x+y'+z)(x+y'+z')(x'+y+z)(x'+y'+z) \\ &= M_2 M_3 M_4 M_6 = \prod (2,3,4,6) \end{aligned}$$

## EXAMPLE 3.4 Conversion to product of maxterms

**PROBLEM** Convert the Boolean function  $F = x'y' + xz$  into the product-of-maxterms form.

**SOLUTION**

$$\begin{aligned} F(x,y,z) &= \sum (0,1,5,7) \\ &\text{minterms } m_0, m_1, m_5, m_7 \text{ from Table} \end{aligned}$$

$$\begin{aligned} F(x,y,z) &= \prod (2,3,4,6) \\ &\text{the missing minterms } m_2, m_3, m_4, m_6 \end{aligned}$$

Truth Table for  
 $F = x'y' + xz$

x	y	z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


## Minterm and Maxterm Expansions

- 3 variables

Row No.	A B C	Minterms	Maxterms
0	0 0 0	$A' B' C' = m_0$	$A + B + C = M_0$
1	0 0 1	$A' B' C = m_1$	$A + B + C' = M_1$
2	0 1 0	$A' B C' = m_2$	$A + B' + C = M_2$
3	0 1 1	$A' B C = m_3$	$A + B' + C' = M_3$
4	1 0 0	$A B' C' = m_4$	$A' + B + C = M_4$
5	1 0 1	$A B' C = m_5$	$A' + B + C' = M_5$
6	1 1 0	$A B C' = m_6$	$A' + B' + C = M_6$
7	1 1 1	$A B C = m_7$	$A' + B' + C' = M_7$

## Minterm and Maxterm Expansions

---
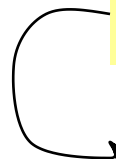
$$f(A, B, C) = m_3 + m_4 + m_5 + m_6 + m_7$$

$$f' = m_0 + m_1 + m_2 = \sum m(0,1,2)$$

$$f(A, B, C) = M_0 M_1 M_2 \longrightarrow f' = \prod M(3,4,5,6,7) = M_3 M_4 M_5 M_6 M_7$$

- *Minterm* and *Maxterm* expansions are complement each other

$$f' = (m_3 + m_4 + m_5 + m_6 + m_7)' = m'_3 m'_4 m'_5 m'_6 m'_7 = M_3 M_4 M_5 M_6 M_7$$

$$f' = (M_0 M_1 M_2)' = M'_0 + M'_1 + M'_2 = m_0 + m_1 + m_2$$

# Combinational Logic Design Using a Truth Table

---


Original equation →

$$f = A'BC + AB'C' + AB'C + ABC' + ABC$$

Simplified equation →

$$f = A'BC + AB' + AB = A'BC + A = A + BC$$

Circuit realization →

 




# Conversion of English Sentences to Boolean Equations

1. The alarm will ring( $Z$ ) iff the alarm switch is turned on( $A$ ) **and** the door is not closed( $B'$ ), **or** it is after 6PM( $C$ ) and window is not closed( $D'$ )

## 2. Boolean Equation

$$Z = AB' + CD'$$

## 3. Circuit realization

 

# From The Truth Table to Algebraic Expressions

- Truth table
  - To find a minimum POS expression
    - Manipulate the previous POS expression to obtain  $f = (A + B + C)(A' + B')$
    - Simplify the SOP expression for  $f'$  and then use DeMorgan to convert it to a POS expression.

Both approaches produce the same result.

- How many different functions of  $n$  variables are there?

a	b	$f_0$	$f_1$	$f_2$	$f_3$	$f_4$	$f_5$	$f_6$	$f_7$	$f_8$	$f_9$	$f_{10}$	$f_{11}$	$f_{12}$	$f_{13}$	$f_{14}$	$f_{15}$
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

Variables	Terms
1	4
2	16
3	256
4	65,536
5	4,294,967,296

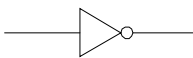
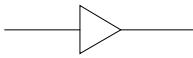
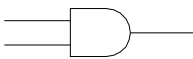
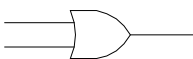
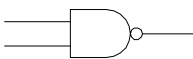
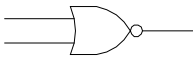

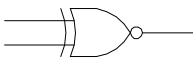
Number of functions of  $n$  variables

# Other logic operations

NAME	OPERATOR SYMBOL	FUNCTION VALUES FOR x,y=				ALGEBRAIC EXPRESSION	COMMENT
		00	01	10	11		
<b>Zero</b>		0	0	0	0	$F_0 = 0$	Binary constant 0
<b>AND</b>	$x \cdot y$	0	0	0	1	$F_1 = xy$	x and y
<b>Inhibition</b>	$x/y$	0	0	1	0	$F_2 = xy'$	x but not y
<b>Transfer</b>		0	0	1	1	$F_3 = x$	x
<b>Inhibition</b>	$y/x$	0	1	0	0	$F_4 = x'y$	y but not x
<b>Transfer</b>		0	1	1	1	$F_5 = y$	y
<b>XOR</b>	$x \oplus y$	0	1	1	0	$F_6 = xy' + x'y$	x or y but not both
<b>OR</b>	$x + y$	0	1	1	1	$F_7 = x + y$	x or y
<b>NOR</b>	$x \downarrow y$	1	0	0	0	$F_8 = (x + y)'$	Not-OR
<b>Equivalence</b>	$x \odot y$	1	0	0	1	$F_9 = xy + x'y'$	x equals y
<b>Complement</b>	$y'$	1	0	1	0	$F_{10} = y'$	Not y
<b>Implication</b>	$x \subset y$	1	0	1	1	$F_{11} = x + y'$	If y, then x
<b>Complement</b>	$x'$	1	1	0	0	$F_{12} = x'$	Not x
<b>Implication</b>	$x \supset y$	1	1	0	1	$F_{13} = x' + y$	If x, then y
<b>NAND</b>	$x \uparrow y$	1	1	1	0	$F_{14} = (xy)'$	Not-AND
<b>One</b>		1	1	1	1	$F_{15} = 1$	Binary constant 1

Boolean Expressions for the 16 Functions of Two Variables

# Basic logic library

NAME	GRAPHIC SYMBOL	FUNCTIONAL EXPRESSION	COST(NUMBER OF TRANSISTORS)	GATE DELAY(NS)	Truth table															
Inverter		$F = x'$	2	1	<table><tr><td>x</td><td>F</td></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	x	F	0	1	1	0									
x	F																			
0	1																			
1	0																			
Driver		$F = x$	4	2	<table><tr><td>x</td><td>F</td></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	x	F	0	0	1	1									
x	F																			
0	0																			
1	1																			
AND		$F = xy$	6	2.4	<table><tr><td>x</td><td>y</td><td>F</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	0	1	0	0	1	1	1
x	y	F																		
0	0	0																		
0	1	0																		
1	0	0																		
1	1	1																		
OR		$F = x+y$	6	2.4	<table><tr><td>x</td><td>y</td><td>F</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	1
x	y	F																		
0	0	0																		
0	1	1																		
1	0	1																		
1	1	1																		
NAND		$F = (xy)'$	4	1.4	<table><tr><td>x</td><td>y</td><td>F</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	1	1	0	1	1	1	0
x	y	F																		
0	0	1																		
0	1	1																		
1	0	1																		
1	1	0																		
NOR		$F = (x+y)'$	4	1.4	<table><tr><td>x</td><td>y</td><td>F</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	0
x	y	F																		
0	0	1																		
0	1	0																		
1	0	0																		
1	1	0																		
XOR		$F = x \oplus y$	14	4.2	<table><tr><td>x</td><td>y</td><td>F</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	0
x	y	F																		
0	0	0																		
0	1	1																		
1	0	1																		
1	1	0																		
XNOR		$F = x \odot y$	12	3.2	<table><tr><td>x</td><td>y</td><td>F</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	1
x	y	F																		
0	0	1																		
0	1	0																		
1	0	0																		
1	1	1																		

# Exclusive-OR and Equivalence Operations

## Exclusive-OR


$$0 \oplus 0 = 0 \quad 0 \oplus 1 = 1$$

$$1 \oplus 0 = 1 \quad 1 \oplus 1 = 0$$

## Truth Table

XY	$X \oplus Y$
0 0	0
0 1	1
1 0	1
1 1	0

## Symbol

 

## Exclusive-OR and Equivalence Operations

---

### Theorems for Exclusive-OR:

$$X \oplus 0 = X$$

$$X \oplus 1 = X'$$

$$X \oplus X = 0$$

$$X \oplus X' = 1$$

$$X \oplus Y = Y \oplus X \text{ (commutative law)}$$

$$(X \oplus Y) \oplus Z = X \oplus (Y \oplus Z) = X \oplus Y \oplus Z \text{ (associative law)}$$

$$X(Y \oplus Z) = XY \oplus XZ \text{ (distributive law)}$$


$$(X \oplus Y)' = X \oplus Y' = X' \oplus Y = XY + X'Y'$$

# NAND, NOR, AND EXCLUSIVE-OR GATES


---
 
## ■ Three other gates

- Exclusive-OR gates.
  - An Exclusive-OR gate





- An Exclusive-NOR gate

 


✓ Exclusive-OR gate implements the expression

  - $(a \oplus b) = a'b + ab'$
- $(a \oplus b)' = a'b' + ab$



# Binary Adders and Subtractors

## Truth Table for a Full Adder

 


$X$	$Y$	$C_{in}$	$C_{out}$	$Sum$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


 
# Full adder

$$\begin{aligned} Sum &= X'Y'C_{in} + X'YC'_{in} + XY'C'_{in} + XYC_{in} \\ &= X'(Y'C_{in} + YC'_{in}) + X(Y'C'_{in} + YC_{in}) \\ &= X'(Y \oplus C_{in}) + X(Y \oplus C_{in})' = X \oplus Y \oplus C_{in} \end{aligned}$$

$$\begin{aligned} C_{out} &= X'YC_{in} + XY'C_{in} + XYC'_{in} + XYC_{in} \\ &= (X'YC_{in} + XYC_{in}) + (XY'C_{in} + XYC'_{in}) + (XYC'_{in} + XYC_{in}) \\ &= YC_{in} + XC_{in} + XY \end{aligned}$$



# Full adder design

## EXAMPLE Full-adder design

**PROBLEM** Design a full adder based on the specifications given in table, using the basic logic library that was given in Table.

The primary goal is to minimize the propagation delay from  $C_i$  to  $C_{i+1}$ , while the secondary goal is to use the smallest possible number of transistors.

## SOLUTION

$$\begin{aligned}
 s_i &= x'_i y'_i c_i + x'_i y_i c'_i + x_i y'_i c'_i + x_i y_i c_i \\
 &= (x'_i y_i + x_i y'_i) c'_i + (x'_i y'_i + x_i y_i) c_i \\
 &= (x_i \oplus y_i) c'_i + (x_i \odot y_i) c_i \\
 &= (x_i \oplus y_i) c'_i + (x_i \oplus y_i)' c_i \\
 &= (x_i \oplus y_i) \oplus c_i
 \end{aligned}$$

$$\begin{aligned}
 c_{i+1} &= x_i y_i c'_i + x_i y_i c_i + x'_i y_i c_i + x_i y'_i c_i \\
 &= x_i y_i (c'_i + c_i) + c_i (x'_i y_i + x_i y'_i) \\
 &= x_i y_i + c_i (x_i \oplus y_i)
 \end{aligned}$$

Addition of Binary Digits

$x_i$	$y_i$	$c_i$	$c_{i+1}$	$s_i$
0	0	0	<b>0</b>	<b>0</b>
0	0	1	<b>0</b>	<b>1</b>
0	1	0	<b>0</b>	<b>1</b>
0	1	1	<b>1</b>	<b>0</b>
1	0	0	<b>0</b>	<b>1</b>
1	0	1	<b>1</b>	<b>0</b>
1	1	0	<b>1</b>	<b>0</b>
1	1	1	<b>1</b>	<b>1</b>

# Full adder design

2B - 42

## ■ Modify the expression (faster, less expensive NAND and NOR gates)


### • De Morgan's theorems :

$$\begin{aligned} c_{i+1} &= x_i y_i + c_i (x_i + y_i) \\ &= ((x_i y_i)' (c_i (x_i + y_i)))' \end{aligned}$$

$$\begin{aligned} s_i &= (x_i \oplus y_i) c_i' + (x_i \odot y_i) c_i \\ &= (x_i \odot y_i)' c_i' + (x_i \odot y_i) c_i \\ &= (x_i \odot y_i) \odot c_i \end{aligned}$$


*In addition, with two NANDs and one OR gates :*
 
$$\begin{aligned} (x_i \odot y_i) &= x_i y_i + x_i' y_i' \\ &= ((x_i y_i)' (x_i' y_i'))' \\ &= ((x_i y_i)' (x_i + y_i))' \end{aligned}$$



# A seven-segment display

## ■ The Development of Truth Tables

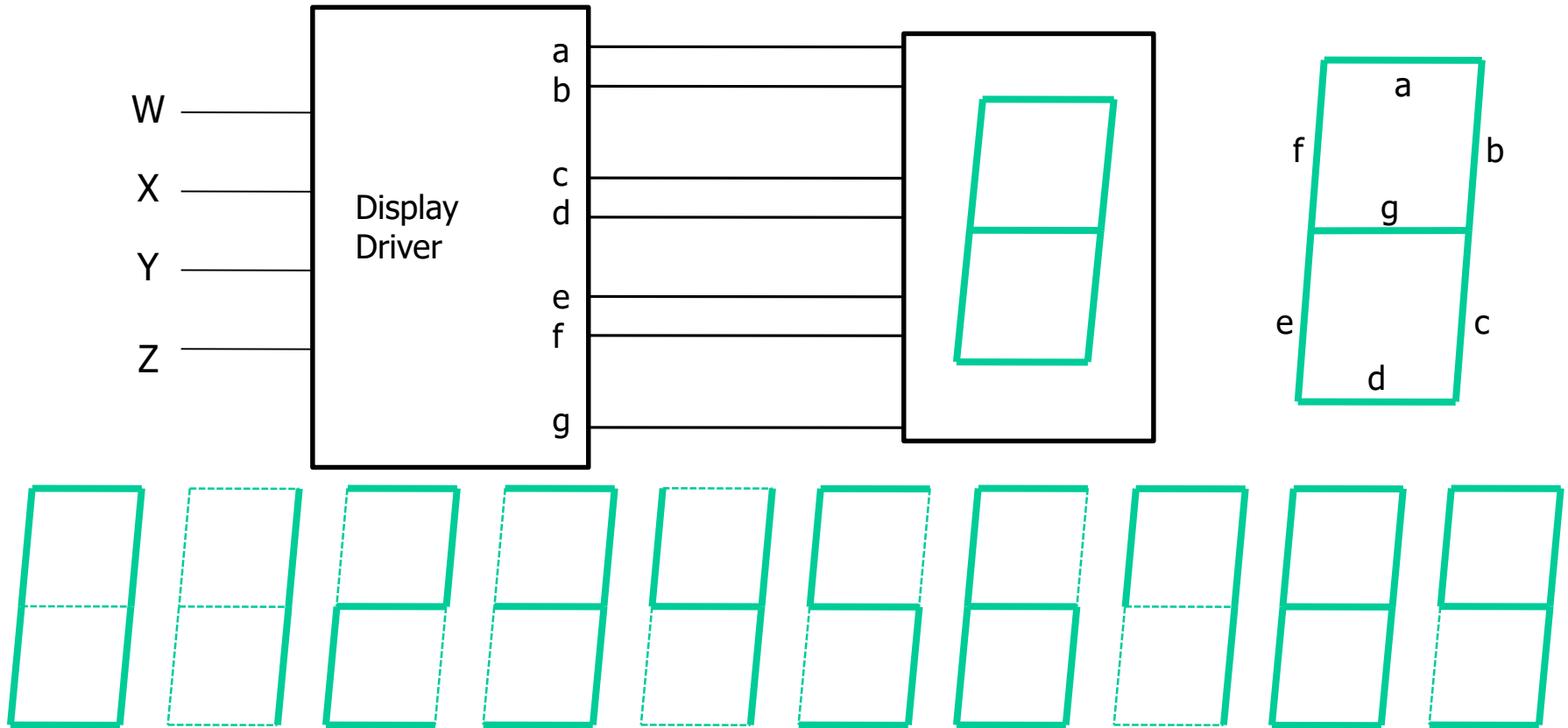

# Truth table for seven segment display

## ■ The Development of Truth Tables

Digit	W	X	Y	Z	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	X	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	X	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	X	0	1	1
-	1	0	1	0	X	X	X	X	X	X	X
-	1	0	1	1	X	X	X	X	X	X	X
-	1	1	0	0	X	X	X	X	X	X	X
-	1	1	0	1	X	X	X	X	X	X	X
-	1	1	1	0	X	X	X	X	X	X	X
-	1	1	1	1	X	X	X	X	X	X	X